

## INTERFACING: Memory and I/O Mapped I/O

### 1. I/O Interfacing Techniques

- Microprocessor, isolates memory and IO system
- It provides instruction for addressing memory and IO system. This is done by  $M/\overline{IO}$  signal in 8085.

$M/\overline{IO} = 1$ ; microprocessor communicating with memory system.

$M/\overline{IO} = 0$ ; microprocessor communicating with IO system.

- In IO addressing mode 8085 has capability of 8 bit IO address, through which it can address 255 IO ports.
- Microprocessor also provides facility to, treat IO devices as memory location. In this case, one can map IO devices in memory map.
- Thus, due to above two methods of interfacing IO devices, we have two techniques of IO mapping i.e.
  1. I/O mapped I/O
  2. Memory mapped I/O

### → I/O Mapped I/O [I/O PORT ADDRESSING]

- In this case the IO device is treated as IO device only
- Each IO device uses eight bits of address line and control signals  $\overline{IOR}$  (Input output read) and  $\overline{IOW}$  (Input output Write)
- The address bus of 8085 microprocessor is of 16 bits, but for IO devices only 8 bits address is used. So to implement this the 8 bit address is transferred on both address groups i.e.  $A_0$  to  $A_7$  and  $A_8$  to  $A_{15}$ .
- The contents available are same, so one can use any one group i.e.  $A_{15}$  to  $A_7$  or  $A_7$  to  $A_0$  or combination

of two groups.

- Let us consider an example if address of I/O device is 50H.

The contents transferred on  $A_0$  to  $A_{15}$  will be as follow:

$A_{15}$	$A_{14}$	$A_{13}$	$A_{12}$	$A_{11}$	$A_{10}$	$A_9$	$A_8$	$A_7$
0	1	0	1	0	0	0	0	0

50

$A_6$	$A_5$	$A_4$	$A_3$	$A_2$	$A_1$	$A_0$
1	0	1	0	0	0	0

50

So we can use 50H address given by  $A_7$  to  $A_0$  or  $A_{15}$  to  $A_7$  or we can use  $A_0$  or  $A_8$ ,  $A_1$  or  $A_9$  and so on  $A_7$  or  $A_{15}$ .

This will be represented as follow:

$A_{7/15}$	$A_{6/14}$	$A_{5/13}$	$A_{4/12}$	$A_{3/11}$	$A_{2/10}$	$A_{1/9}$	$A_{0/8}$

- The above representation specifies that line contents are same. So to address an I/O device we can use  $A_0$  or  $A_8$ .
- There are two special instructions available for data transfer b/w an I/O device and microprocessor.  
In I/O mapped I/O:

(1) IN address

(2) OUT address.


### INPUT OUTPUT INTERFACING IN I/O MAPPED I/O


- The address for I/O devices is of 8 bits, so  $2^8 = 256$  I/O devices can be connected to system.



 (2)

- For input device we require  $\overline{IOR}$  signal and for output device  $\overline{IOW}$  signal. As with  $\overline{IOR}$  and  $\overline{IOW}$  one can differentiate between input and output devices, so even if both the devices have same address there will be no problem.
- The number of devices which can be connected are 256 input and 256 output devices.
- Now to interface these devices to 8085, the control pins of I/O devices should be synchronised with 8085.
- The input device control pins  $\overline{TG}$  and  $\overline{2G}$  should be connected to combination of address and control signal  $\overline{IOR}$ . When  $\overline{TG}$  and  $\overline{2G}$  are active the buffer will get enabled and transfer data on to the data bus.
- Similarly for output device we connect  $\overline{OC}$  to ground and use enable  $\overline{G}$  input to control the latch. So the  $\overline{G}$  input is connected to combination of address and control signal  $\overline{IOW}$ .
- The interfacing of input and output device will be as shown



 

### Input Output interfacing in IO mapped I/O



- The interfacing diagram is divided in two separate parts:
  - 1) for input device i.e. buffer
  - 2) for output device i.e. latch.
- For both the interfacing diagrams combination of address lines is done by 8 input NAND gate. The address lines used are  $A_0$  to  $A_7$  (or we can use  $A_8$  to  $A_{15}$ ).
- When the combination of input get satisfied the output will be low and for all other combinations it will be high. This output is then combined with control signal  $\overline{IOR}$  or  $\overline{IOW}$  to generate signals to enable buffer and latch.
- The output of buffer is connected to data bus and input of latch is connected to data bus.
- The address of input and output device is calculated from combination of address lines as follows:
 

Input device = 1111	1111 = FFH
Output device = 1111	1110 = FEH
- Instead of logic gates a decoder logic can be used to do the same function. When the decoder logic is used from its many outputs one of the output is used to enable one device.
- The general interfacing of I/O device is shown.




The two cases of address selection logic:

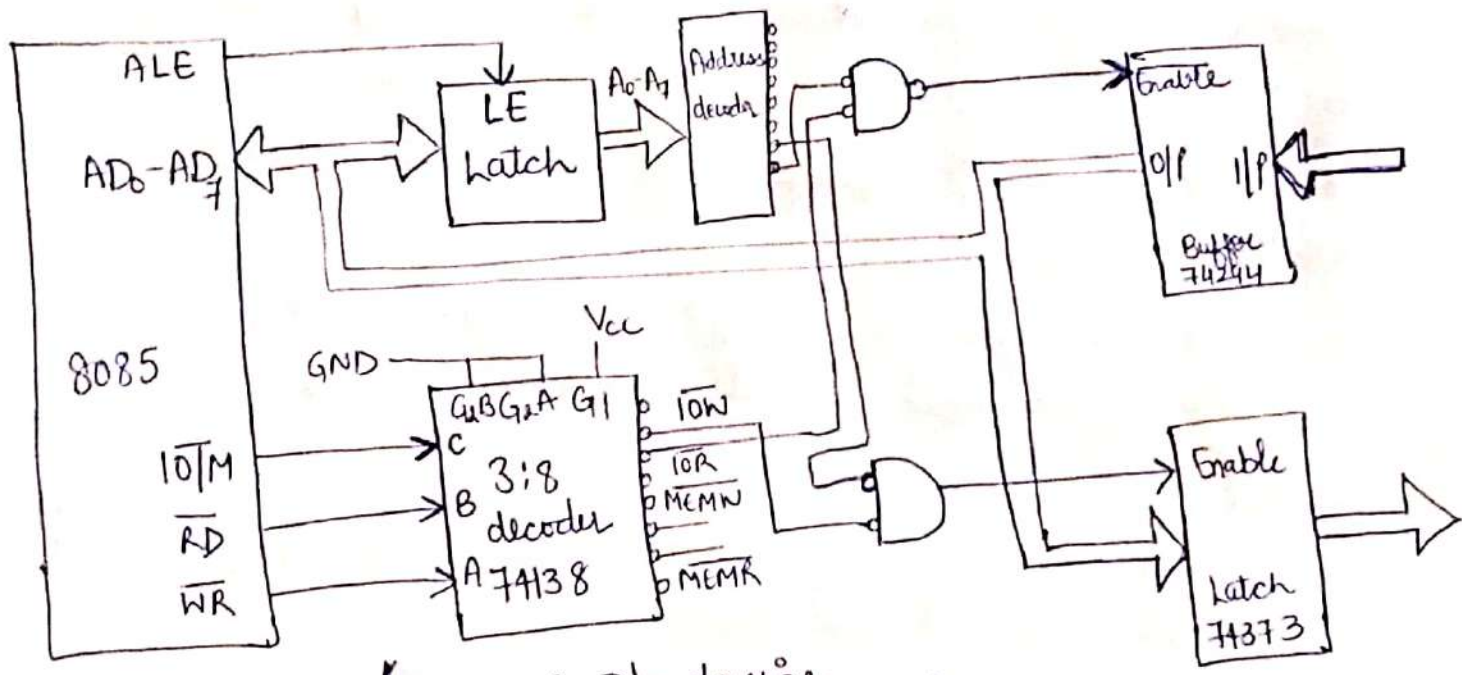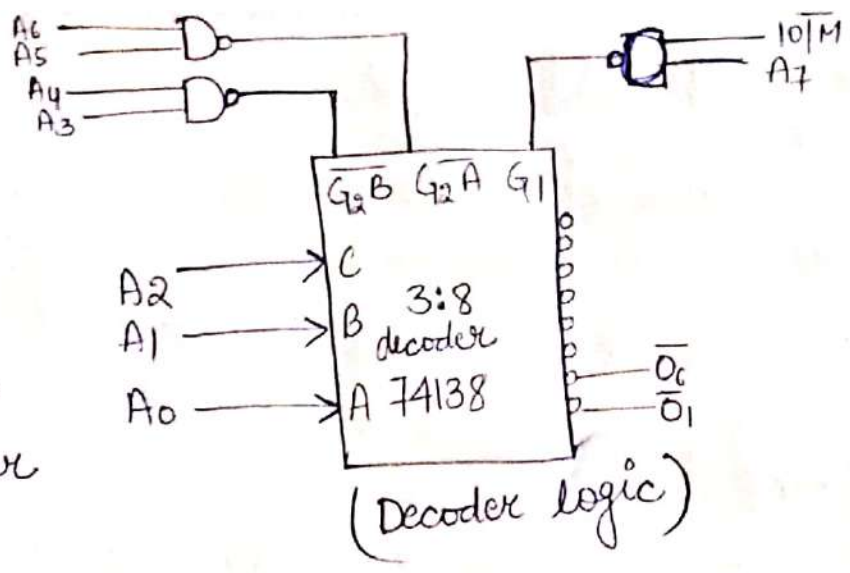- (1) Using logic gates
  - (2) Using 3:8 decoder
- are shown



(General I/O device interfacing)

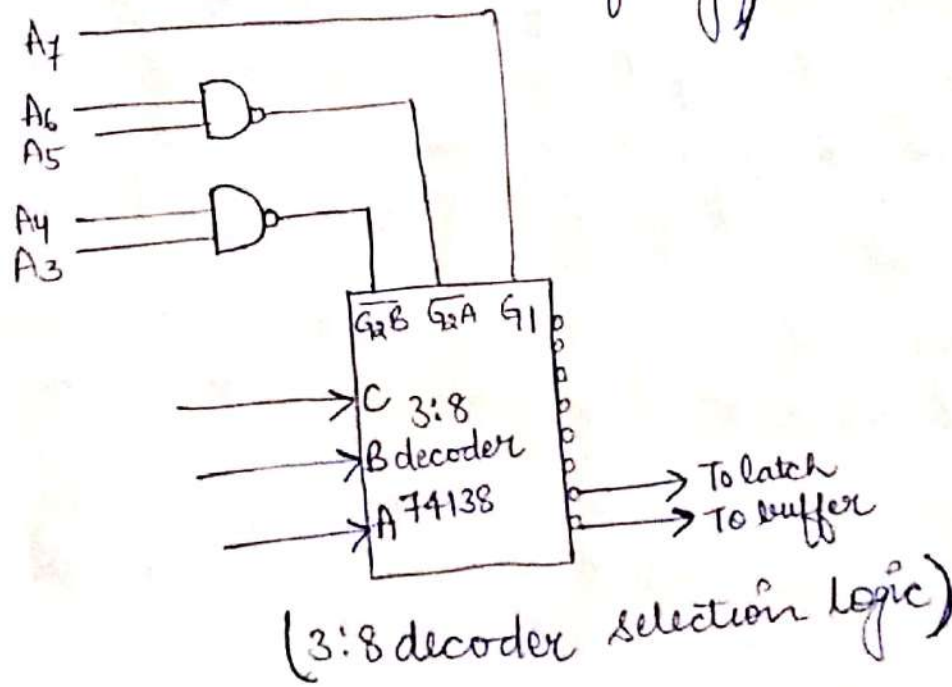


## → MEMORY MAPPED I/O

- In this case the I/O device are treated as memory location. There will be no separation like memory or I/O.
- Each device (I/O) will have 16 bit address.
- The control signals used will be same as memory i.e.  $\overline{\text{MEMR}}$  and  $\overline{\text{MEMW}}$ .
- The interfacing between the I/O and microprocessor will be same as single memory location. Because of this the instructions for I/O device will be memory related instruction for ex. LDA, STA, LDAX, STAX, MOVA etc.
- The number of I/O device will be 64KB shared by I/O and memory.
- For data transfer, microprocessor will send address on  $A_0$  to  $A_{15}$  lines and generates control signals or  $\overline{\text{MEMR}}$  and  $\overline{\text{MEMW}}$ .
- In  $\overline{\text{MEMR}}$  it accept data from I/O device while in  $\overline{\text{MEMW}}$  it transfer data to I/O device.
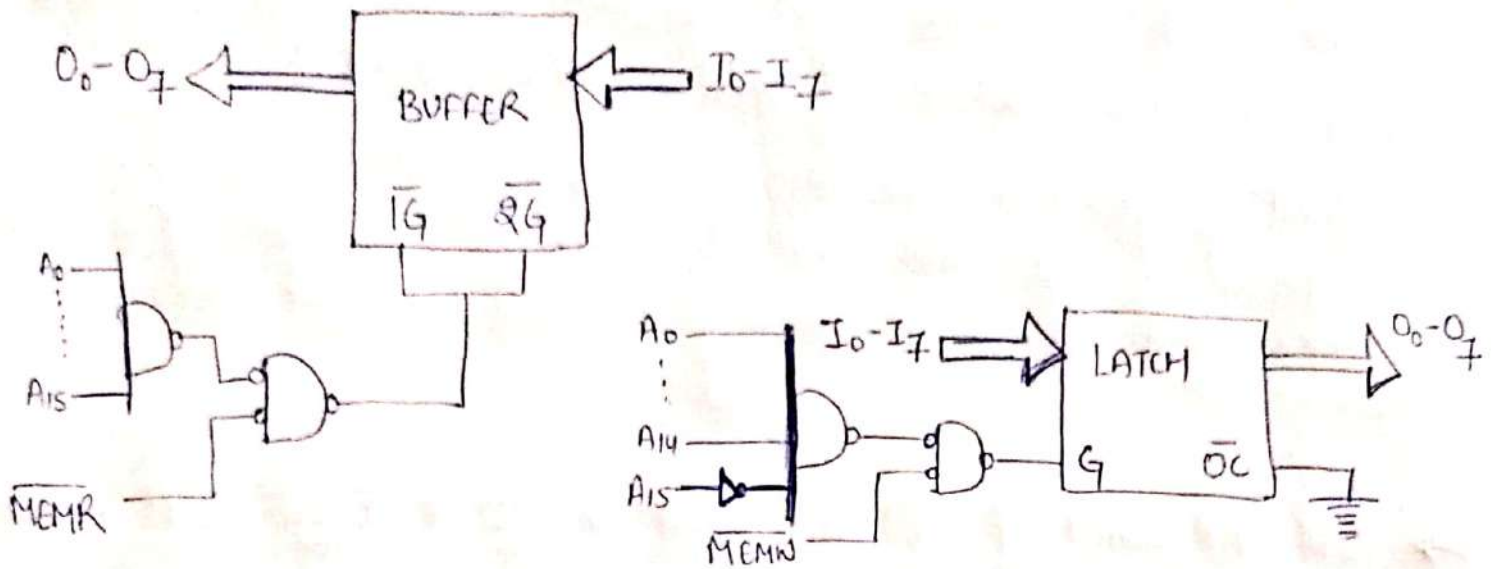
### INPUT/OUTPUT INTERFACING IN MEMORY MAPPED I/O


- The simple input output device is a buffer and output device is latch. To interface these devices to 8085, the control lines  $\overline{\text{TG}}$ ,  $\overline{\text{2G}}$  of buffer and  $\overline{\text{G}}$  input of latch is controlled from 8085.
- The address is of 16 bits  $A_0$  to  $A_{15}$  and control signal  $\overline{\text{MEMR}}$  and  $\overline{\text{MEMW}}$  are used to control the buffer latch.
- The combination of address lines  $A_0$  to  $A_{15}$  can be done by using NAND gates and then it is combined with  $\overline{\text{MEMR}}$  and  $\overline{\text{MEMW}}$  signal.
- The interfacing diagram is




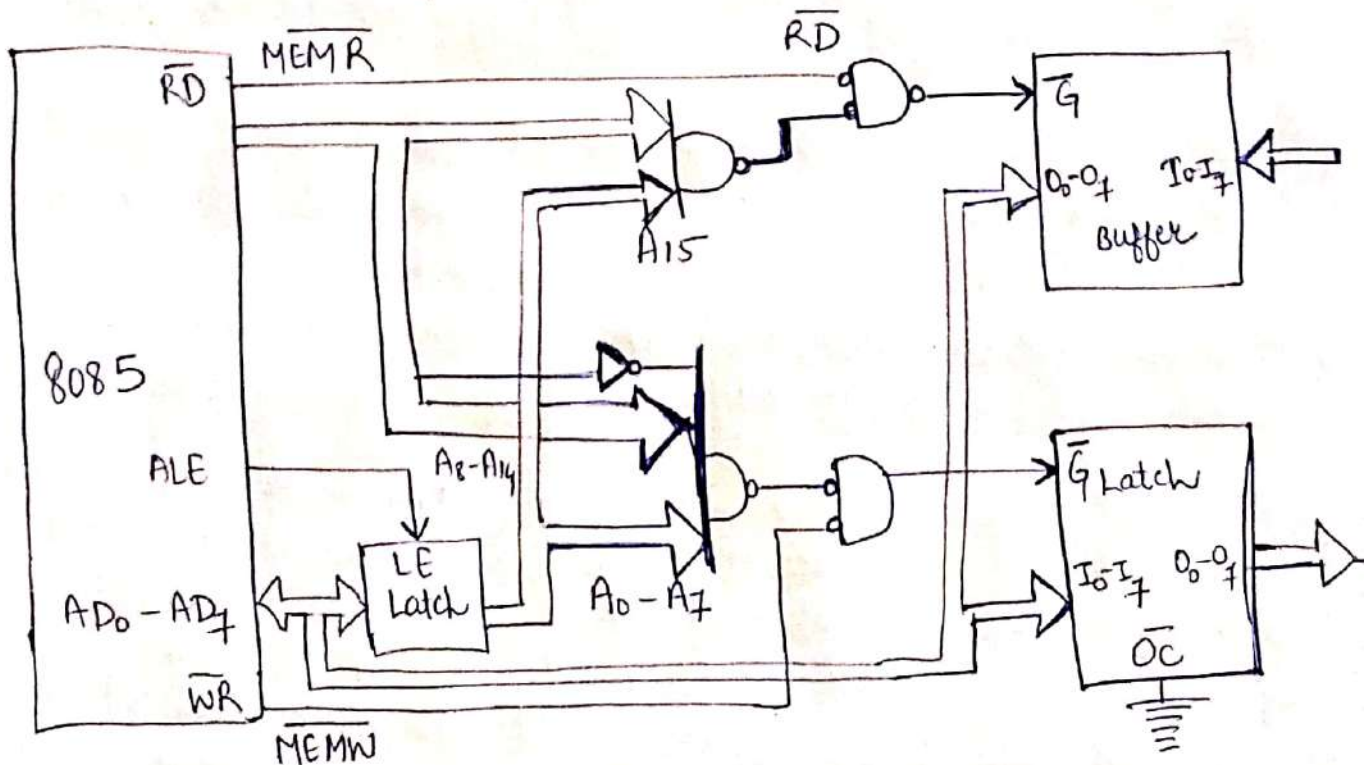
## (Input/output interfacing in memory mapped I/O)

For buffer when  $A_0$  to  $A_{15}$  are all 1's the output of NAND gate will be low. It is then combined with  $\overline{MEMR}$  using NAND gate with inverted inputs and connected to 1G and 2G. So the address of buffer will be FFFF H.



- For latch when  $A_0$  to  $A_{14}$  all are 1's and the line  $A_{15} \overline{MEMW} = 0$  the output of NAND gate will be low, it is then combined with  $\overline{MEMW}$  using AND gate with inverted inputs and connected to  $\overline{G}$ , so the address of latch will be  $7FFFH$ .
- Instead of gates a 3:8 decoder logic can be used to select appropriate device. The general interfacing diagram of an I/O device with 8085 in memory mapped I/O scheme is shown.

### → COMPARISON OF MEMORY MAPPED I/O AND I/O MAPPED I/O

I/O Mapped I/O	Memory mapped I/O
<ol style="list-style-type: none"> <li>1. I/O devices are treated as I/O and memory as memory.</li> <li>2. Device address is 8/16 bits.</li> <li>3. Control signals used for I/O are <math>\overline{IOR}</math> and <math>\overline{IOW}</math>.</li> <li>4. Special instructions are available such as IN and OUT.</li> <li>5. Data transfer is possible b/w accumulator and I/O only.</li> <li>6. The total devices which can be connected will be 1MB memory and maximum 65,535 Input &amp; maximum 65,535 out.</li> <li>7. The arithmetic and logical operations are not possible with direct data from I/O device.</li> </ol>	<ol style="list-style-type: none"> <li>1. Both the devices i.e I/O and memory are treated as memory.</li> <li>2. Device address is 20 bits.</li> <li>3. Control signals used for I/O are <math>\overline{MEMR}</math> and <math>\overline{MEMW}</math>.</li> <li>4. All memory related instruction can be used to communicate with I/O.</li> <li>5. Data transfer is possible b/w any register and I/O.</li> <li>6. The total devices will be only 1MB as it is shared b/w memory and I/O.</li> <li>7. The arithmetic and logical operations can be performed on direct data from I/O device.</li> </ol>